

22. I Producing Electric Current
- When two conducting spheres touch, charges flow from a higher potential to a lower potential
 - Flow of charged particles = electric current
 - conventional current (+) flows in opposite direction to electrons
 - Voltaic or galvanic cell (common dry cell) transforms chemical $e \rightarrow$ electrical e
 - Several galvanic cells = battery
- II Electric circuits
- Any closed loop or conducting path allowing electrical charges to flow = electrical current
 - Conservation of charge
 - charges cannot be created nor destroyed
- III Rates of Charge Flow + Energy Transfer
- Electric currents measured in coulombs per second (C/s) \rightarrow A
 - represented by I (amperage)

www.connected.mcgraw-hill.com

YSEP-6PLZ-4J00

Jan 1-5:04 PM

- IV Diagramming Circuits
- Ammeter measures current, voltmeter measures potential difference (or) \rightarrow Figure 6 (p. 1414) for symbols
 - Ammeter should be connected so current goes through ammeter
 - Problem solving strategies (p. 1416) \rightarrow steps 1-5
- V Resistance and Ohm's Law: $R = \frac{AV}{I}$
- The measure of how strongly an object or material impedes current produced by a potential difference = resistance
 - A device having constant resistance independent of potential difference obeys Ohm's law
 - Wires used to connect electrical devices have resistance
 - 4 things affect resistance of a wire
 - length, cross-sectional area, temperature, and kind of metal
 - Controlling Current
 - Current can be controlled by two ways: varying AV and R \rightarrow Figure 8, p 1421
 - Variable Resistors
 - A potentiometer is a variable resistor used to obtain a smooth, continuous variation of current
- VI Parallel and Series Connections
- When a voltmeter is connected "across another component" it is a parallel connection between the voltmeter and circuit
 - Parallel connection - anytime there is two or more paths to follow in a circuit

Jan 3-1:08 PM

22.1 Review

Grade: 12th
Subject: Physics
Date: 1/7/13

Jan 1-5:04 PM

1 Ampere is a unit of _____.

- A potential difference
- B electric current
- C potential energy
- D power

$$I = \frac{\Delta V}{R}$$

Jan 4-8:53 AM

2 A battery can be used to convert _____ energy to electrical energy.

- A electric current
- B electrons
- C chemical energy
- D metal particles

Jan 4-8:53 AM

3 What will the ammeter read in a circuit where $V = 24 \text{ V}$ and $R = 4 \text{ Ohms}$

- A 12 A
- B 24 A
- C 4 A
- D 6 A

Jan 4-9:00 AM

4 The words voltage across are associated with a _____ connection.

- A parallel
- B voltmeter
- C series
- D ammeter

Jan 4-9:01 AM

5 In a electric circuit diagram, the direction of current flow is _____.

- A from the positive terminal
- B from the negative terminal
- C toward the resistor
- D away from the resistor

Jan 4-9:03 AM

- ## 22.2 Electrical Energy in Use
- ### I. Electrical Energy, Resistance, and Power
- A. Energy supplied to a circuit can be transformed in many useful ways
 - B. Heating a resistor
 1. Current moving through a resistor energy because flowing electrons bump into the atoms in the resistor
 2. How much a resistor resists flow of current determines the amount of heat produced
 1. Amount of heat possible to generate is determined by the power of the appliance
 2. $P = I^2 \cdot R$

Jan 4-8:50 AM

- C. Power and Thermal Energy
 1. $P = \frac{(AV)^2}{R}$
 2. Total energy converted thermal energy can be written 3 ways:
 $E = P \cdot t$, $E = I^2 \cdot R \cdot t$, $E = \frac{AV^2}{R} \cdot t$
 - D. Superconductor - a material with zero resistance
- ### II Providing Electrical Energy
- A. To reduce energy lost to heat when transmitting energy long distances (from a dam), current (I) or resistance (R) must be reduced
 1. Total increases with length of wire
 - B. Electric transmission lines
 1. Wasted energy (electrical energy converted to thermal energy) is minimized by resistance being reduced
 - a. can be achieved by using cables (wires) with high conductivity and large diameter
 - b. minimizing the current reduces waste (low amps = less waste)
 2. Long-distance transmission lines always operate voltages higher than household voltages in order to reduce power ($I^2 R$) loss
 - C. Kilowatt-hour = 1000 watts per hour to measure amounts of energy sold commercially
 $\rightarrow 1000W \text{ per } 3600s(1h) \text{ or } 3.6 \times 10^6 J$

Jan 8-1:01 PM

22.2 Review

Grade: 12th
Subject: Physics
Date: 1/8/13

Jan 8-11:27 AM

- 1 A heating coil has a resistance of 100 Ohms. It is designed to operate on 120 V. What is the power consumed by the heating coil (answer in Watts)?

$$\frac{120^2}{100}$$

144 Watts

Jan 8-11:33 AM

2 How much energy, in joules, does a 100-W lightbulb use in 20 s?

$$E = P \cdot t$$

$$100 \cdot 20 = 2,000$$

Jan 8-11:34 AM

3 Why are superconductors often impractical?

- A they are too expensive
- ~~B~~ they are too large for everyday use
- ★ C they must be kept at low temperatures
- D there are no superconducting materials available today

Jan 8-11:36 AM

4 What is the unit of power that commercial energy companies use to measure energy sold?

- A ohms
- B kilowatt-hour
- C joules
- D amperes

Jan 8-11:37 AM

5 What is the thermal energy supplied in one minute by an appliance with a power dissipation of 1.2 kW (answer in kilojoules (kJ))?

$$1.2 \text{ kW} \cdot 60 \text{ s} = 72 \text{ kJ}$$

$$1200 \text{ W} \cdot 60 \text{ s} = 72,000 \text{ J}$$

Jan 8-11:39 AM